
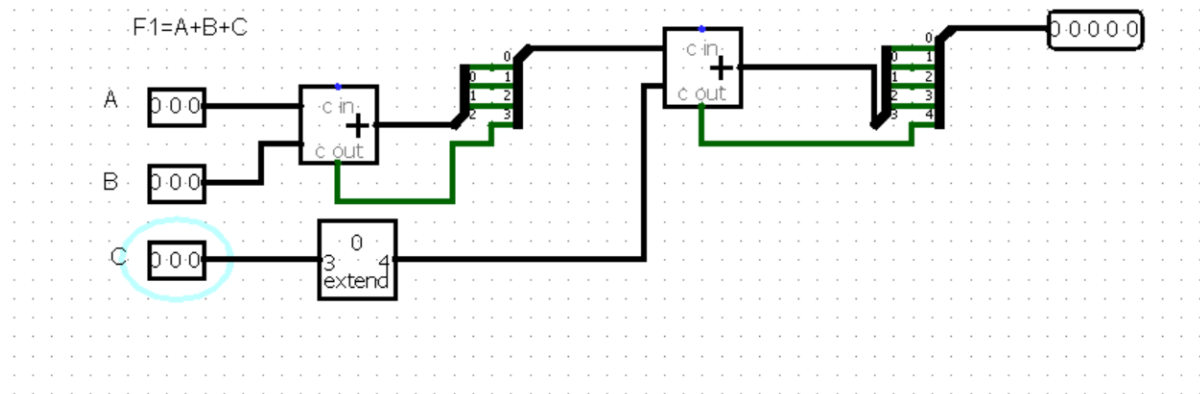


Part 1: Implementation of the components separately

$$F1 = A + B + C$$

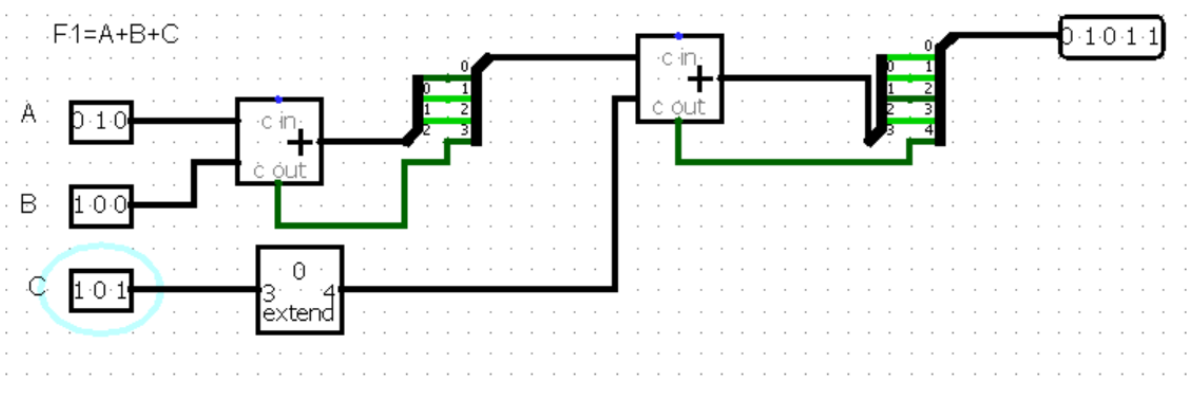

Testing of function F1 is given below:




This testing is correct as the answer is same when it was executed manually.


$$\begin{array}{r} 010 \\ +100 \\ \hline 110 \end{array}$$

$$\begin{array}{r} 110 \\ +101 \\ \hline 1011 \end{array}$$

$$F2 = A - B - C$$

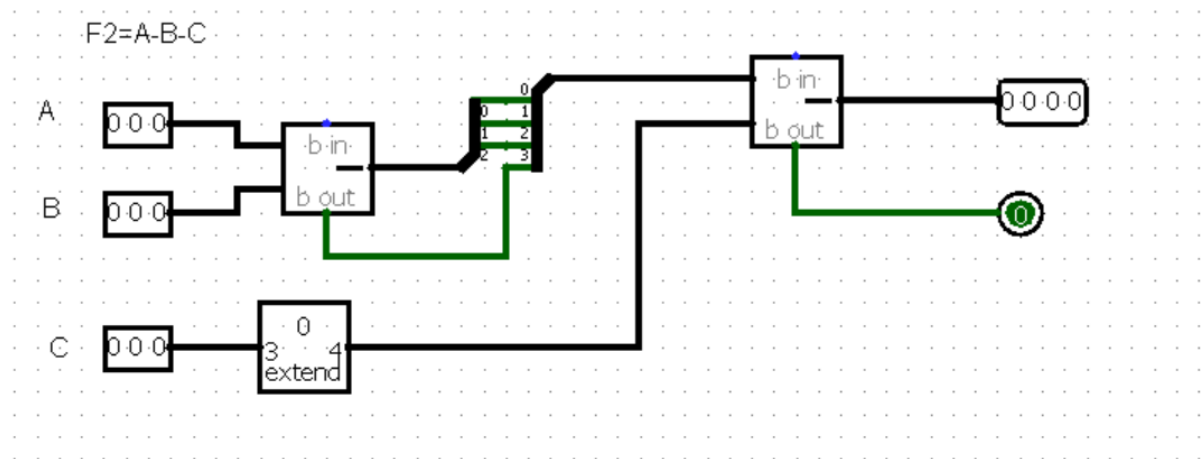

Testing of function F2 is given below:

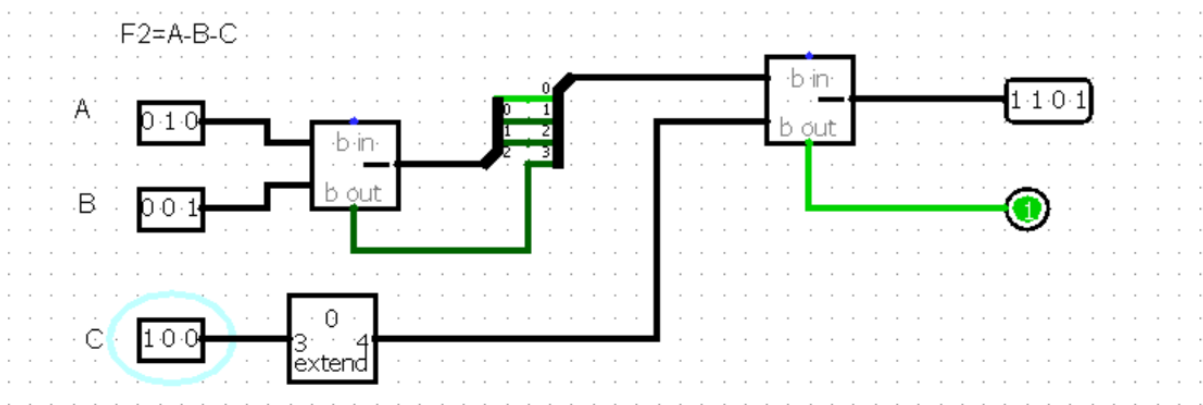

This testing is correct as it gave same result when it was executed manually.

010

-001 = 110 (Complemented the small number)

+1

111

+010

1001 1001

-100 = 1011 (Complemented the small number)


+1

1100


+001

1101


F3= 2's complement of B

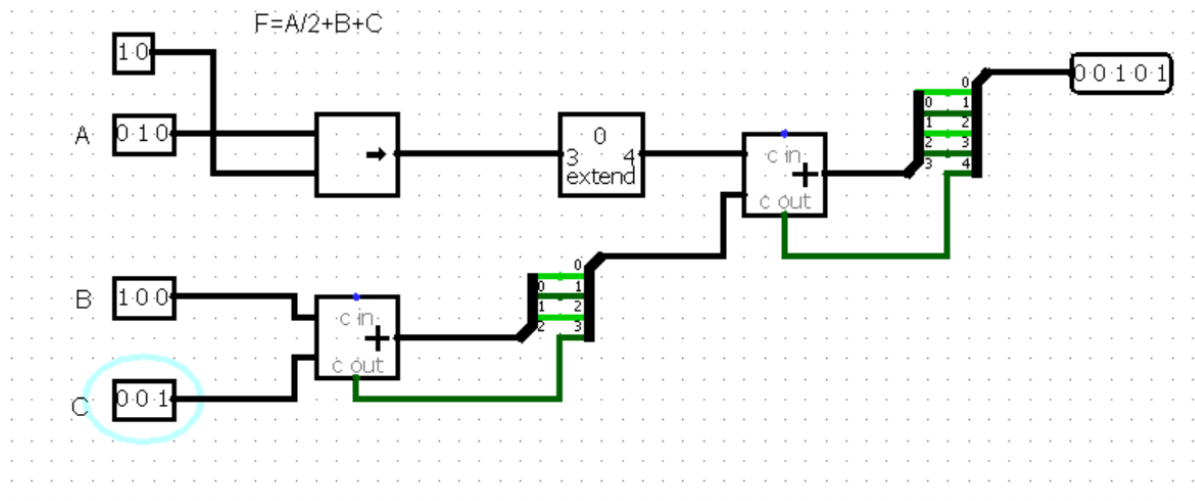


$F5 = A * 4 + B + C$

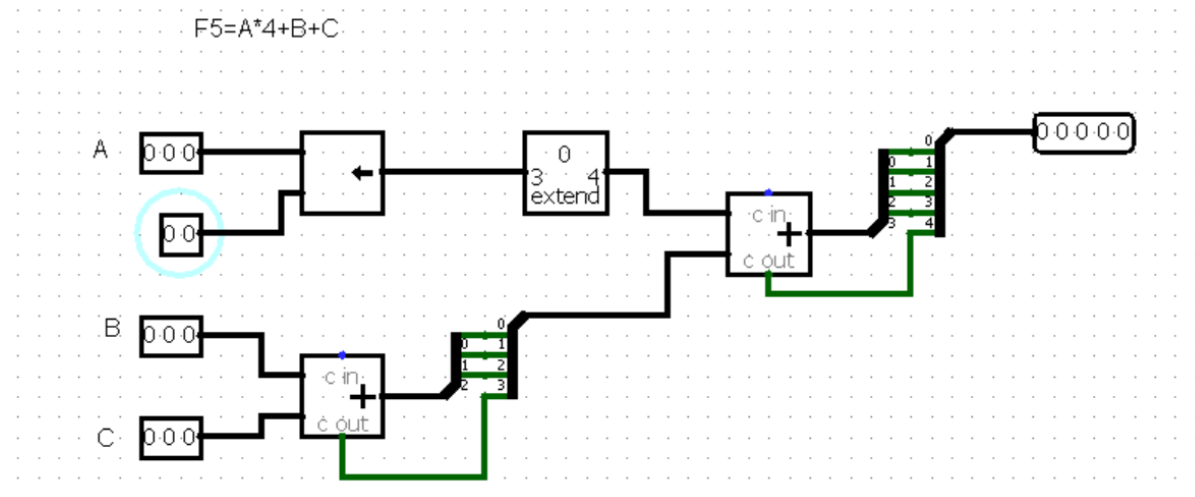


Testing of function F5 is given below:

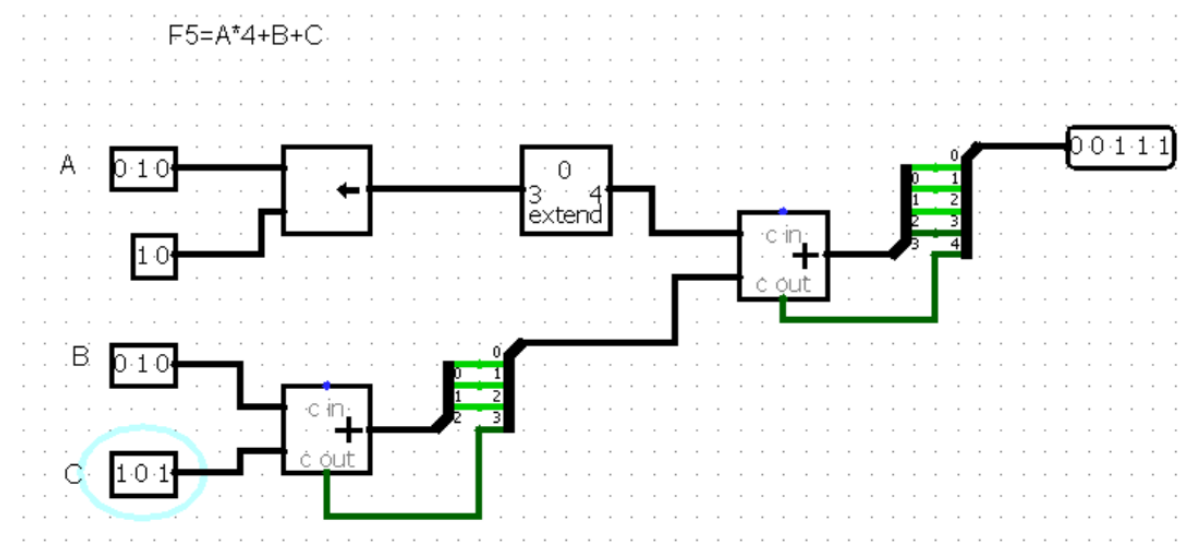


Part 2: Integration of all five components to build an ALU

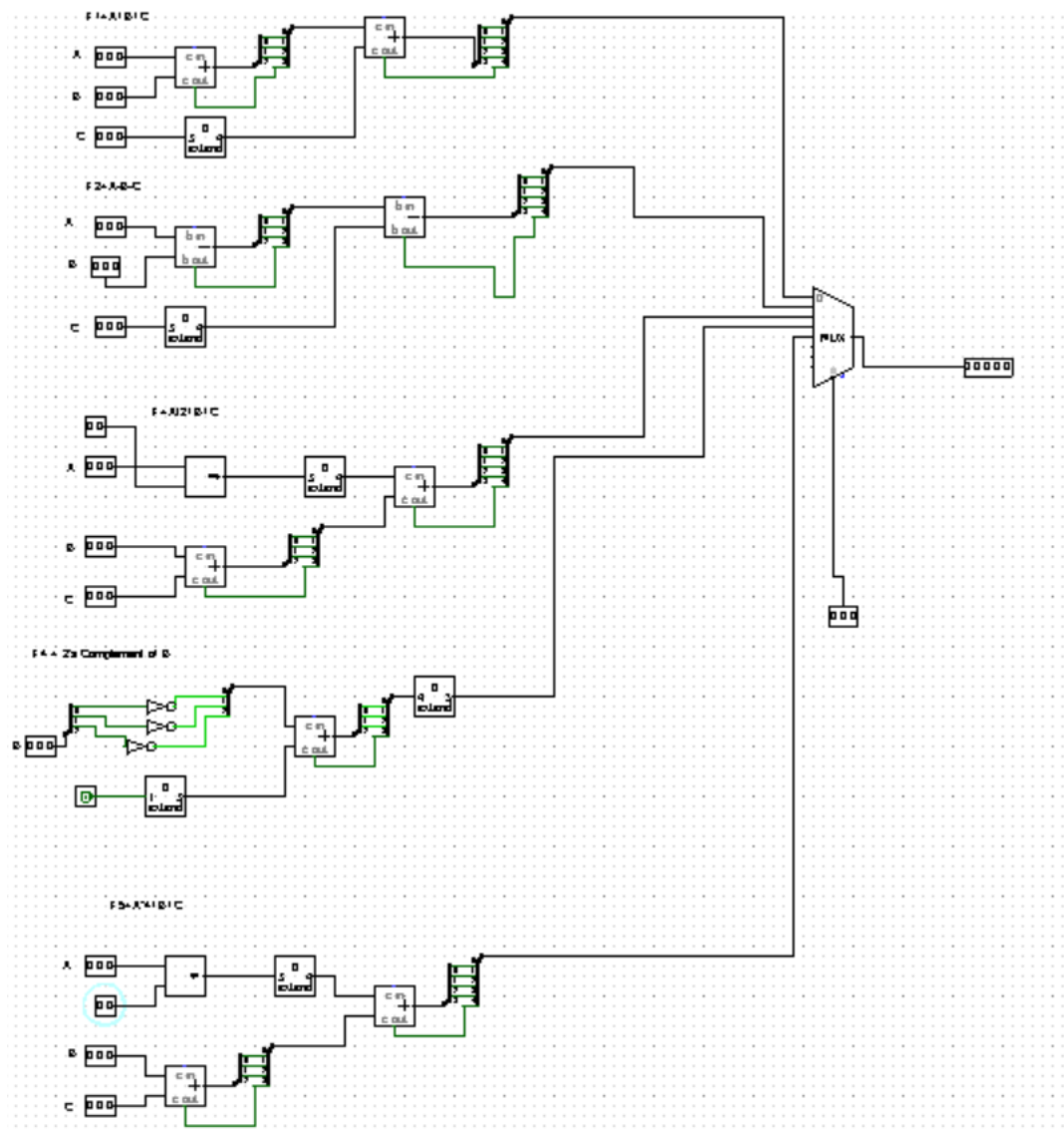


Testing 1:

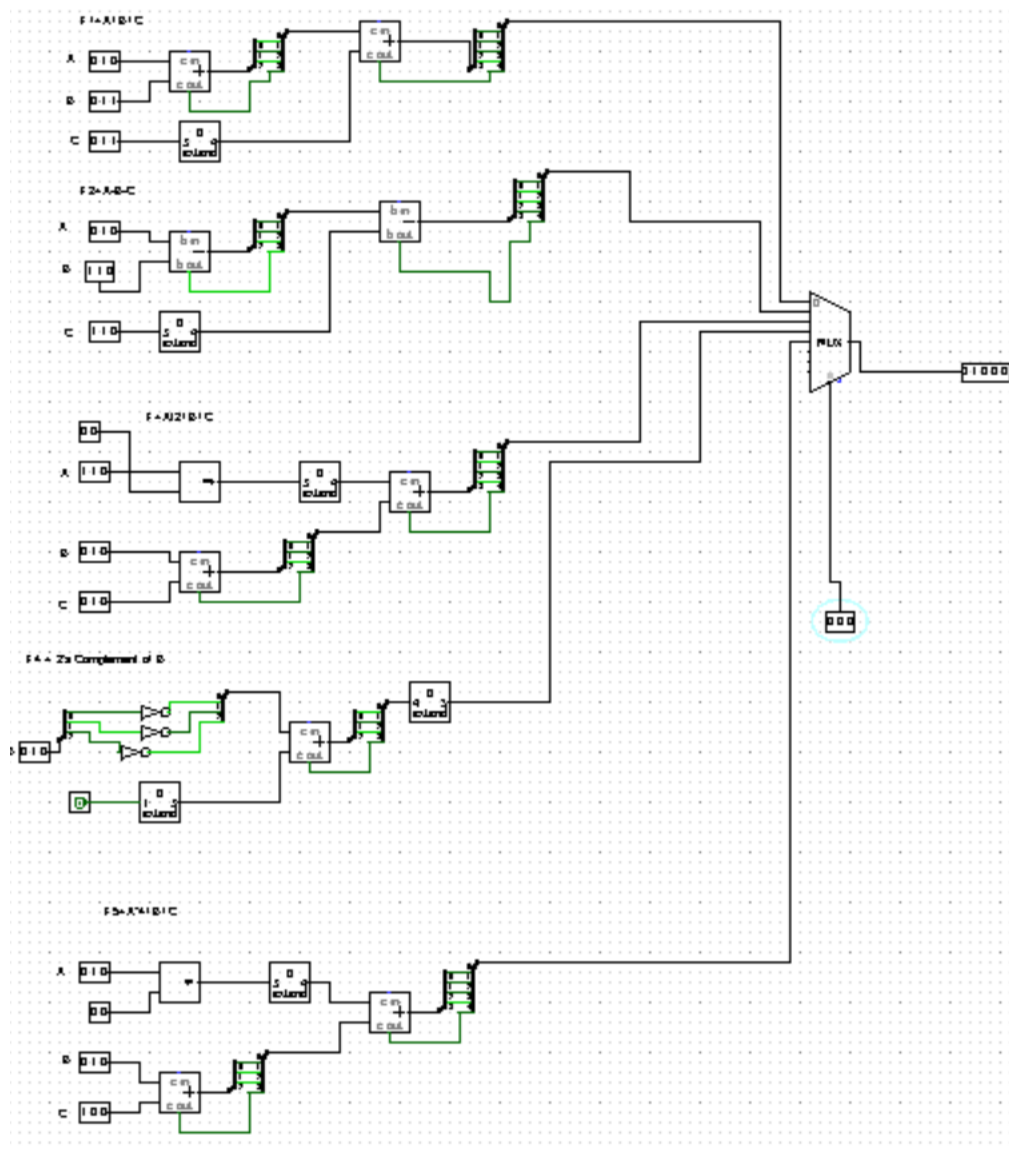


Testing 2:

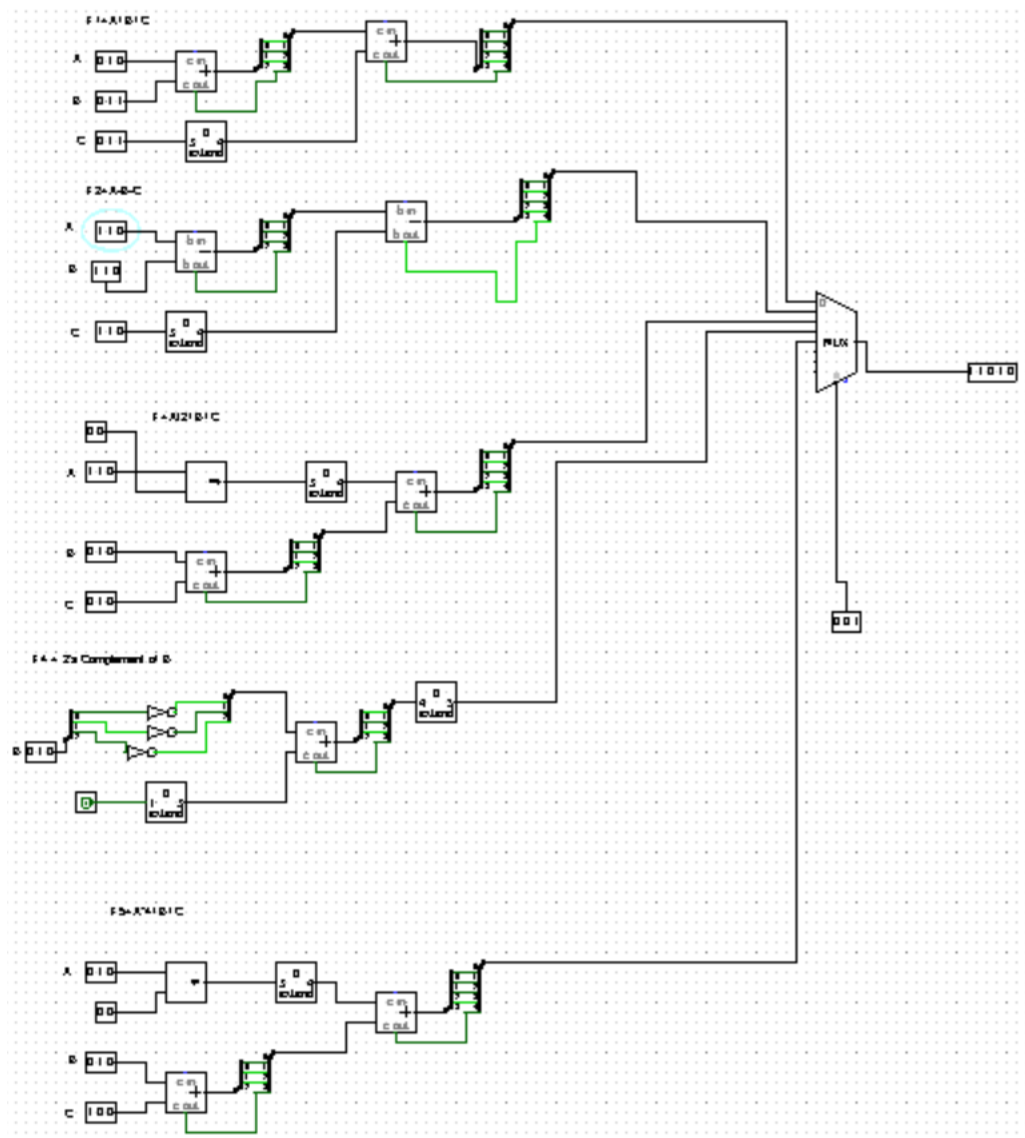


Testing 3:

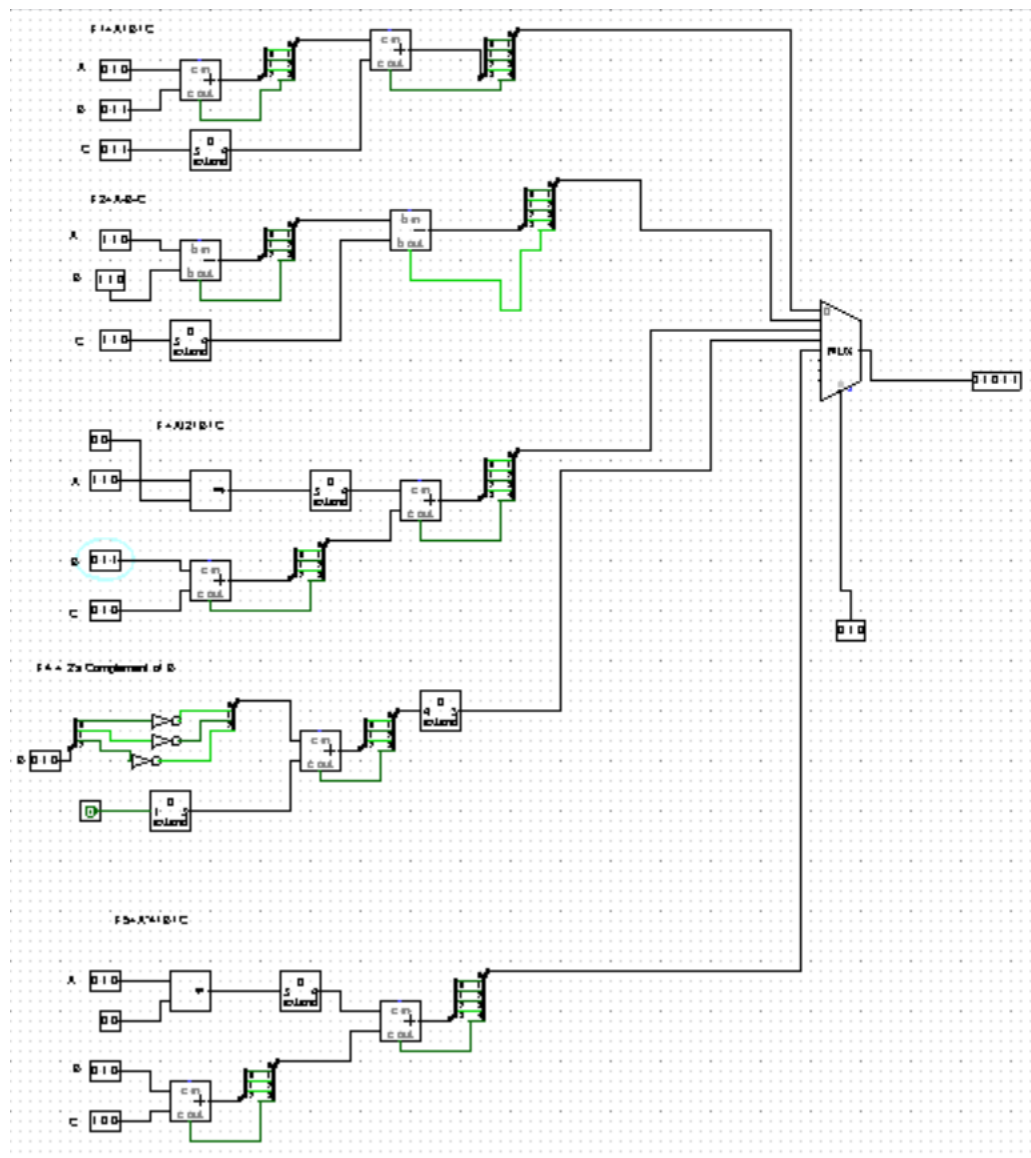


Testing 4:

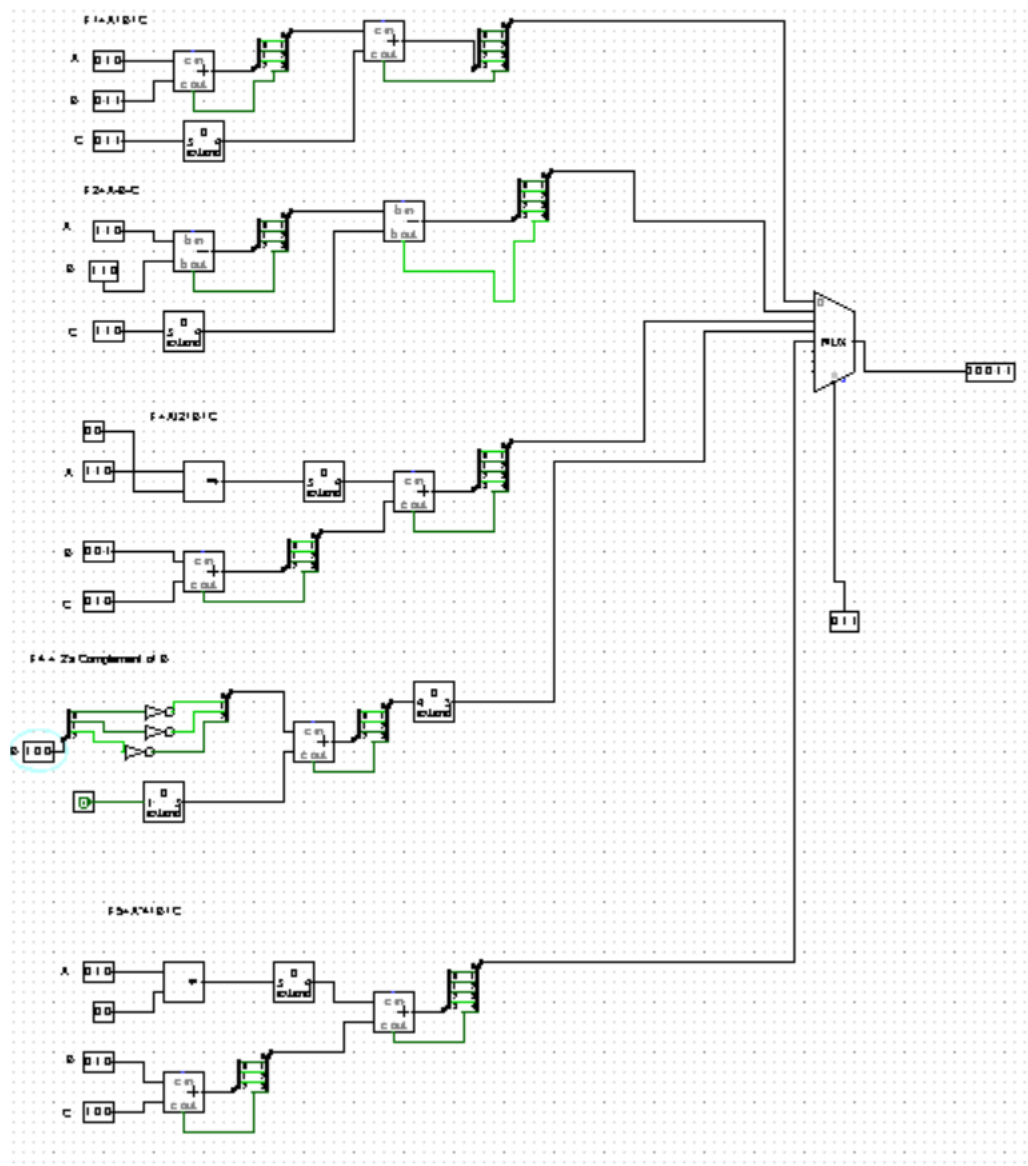


Testing 5:

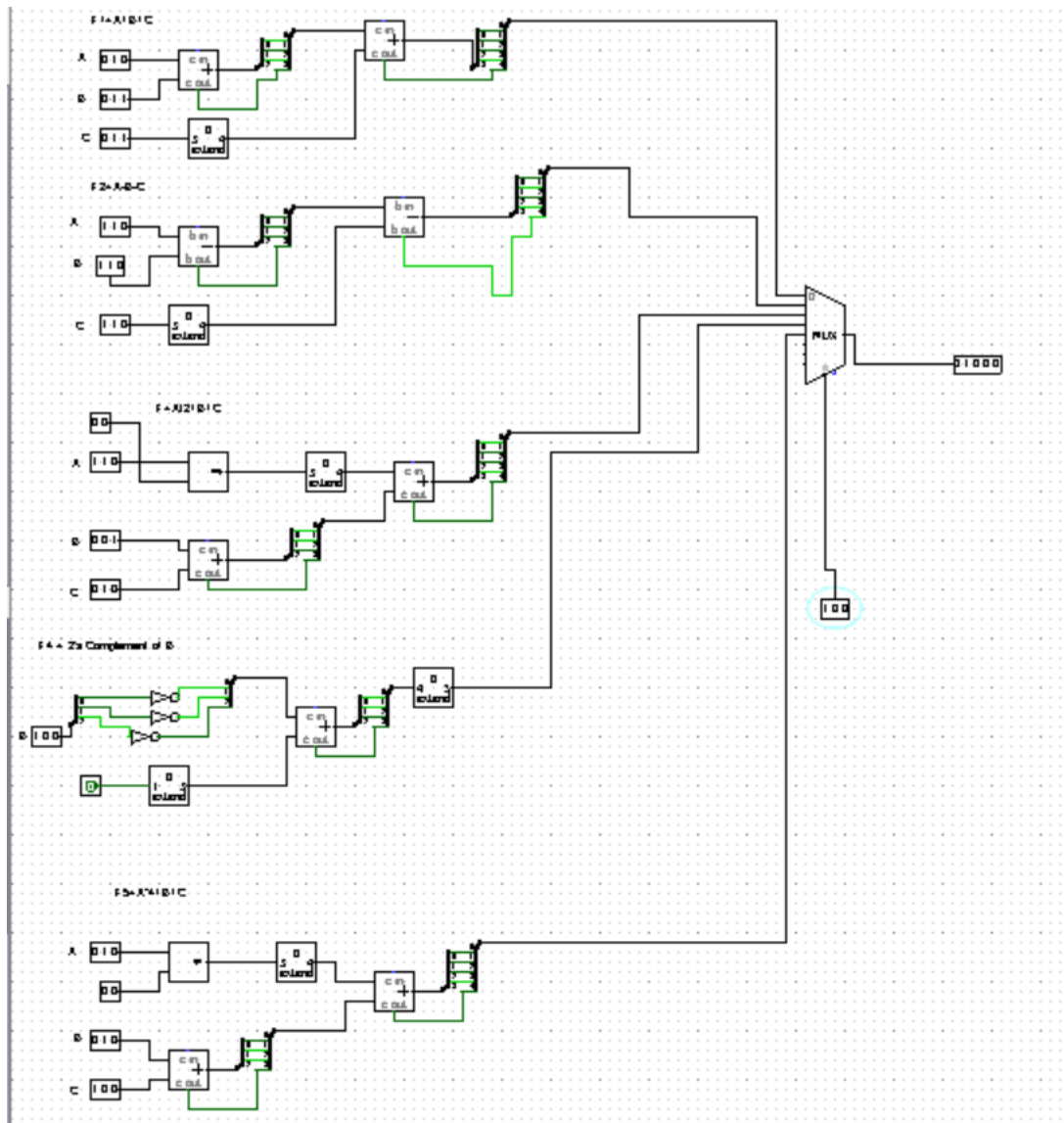

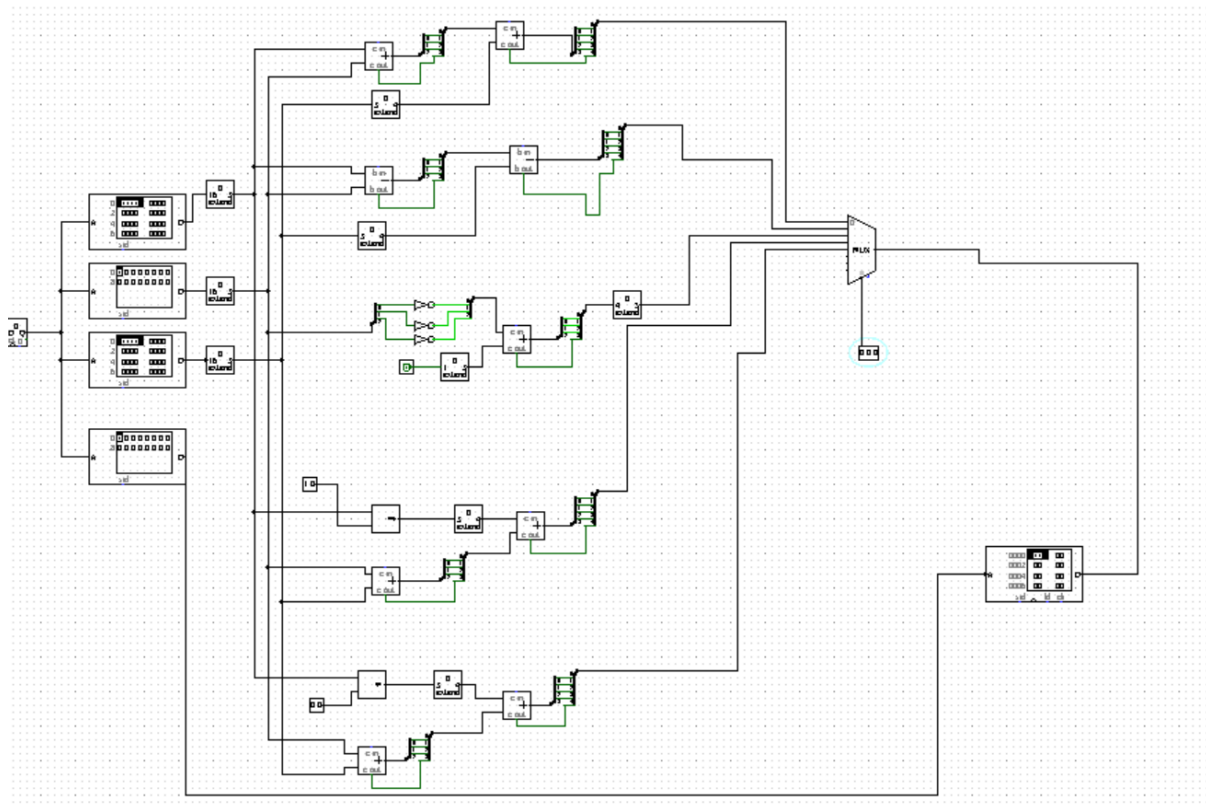Part 3: A toy computer built using ALU, inbuilt ROMs and RAM:




Testing of part 3 is given below:

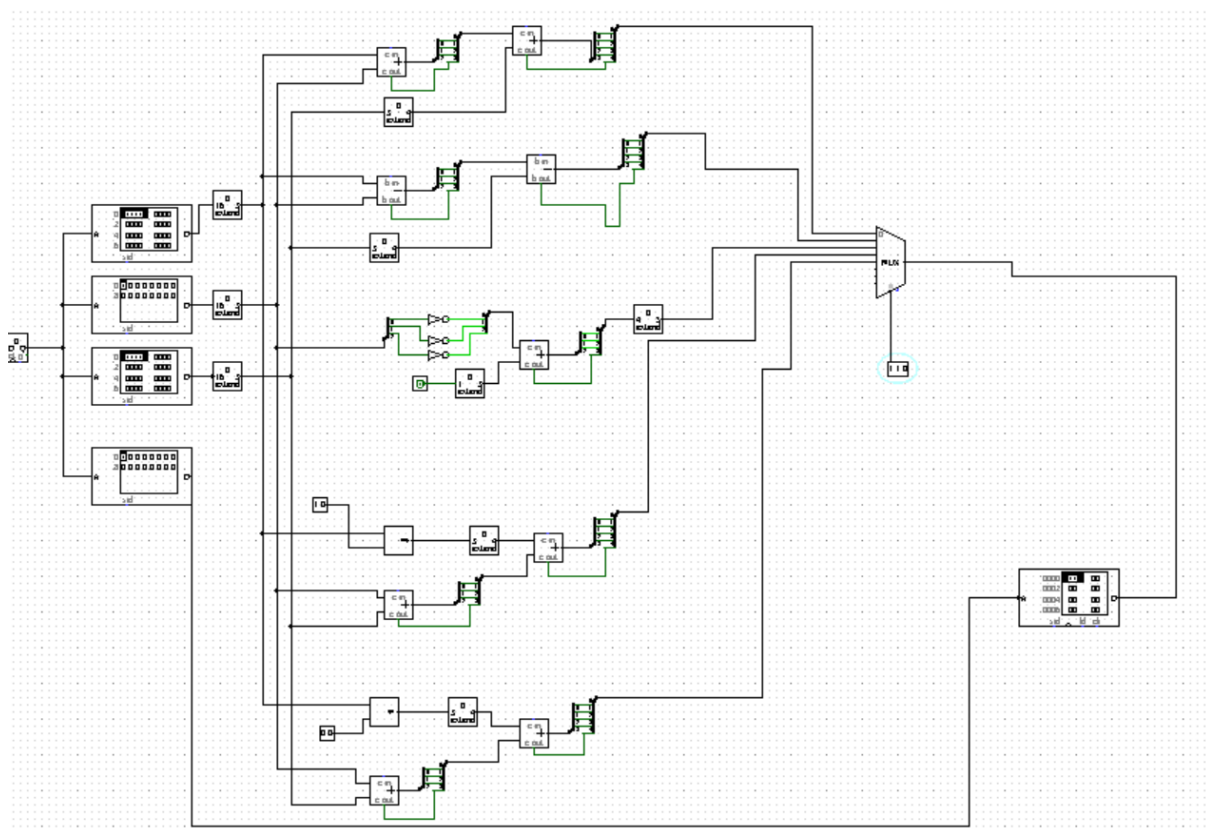


Creation of General Purpose Computer using ALU :

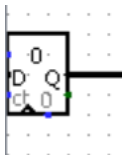
To create a general purpose computer, at first a 4-bit counter was taken:



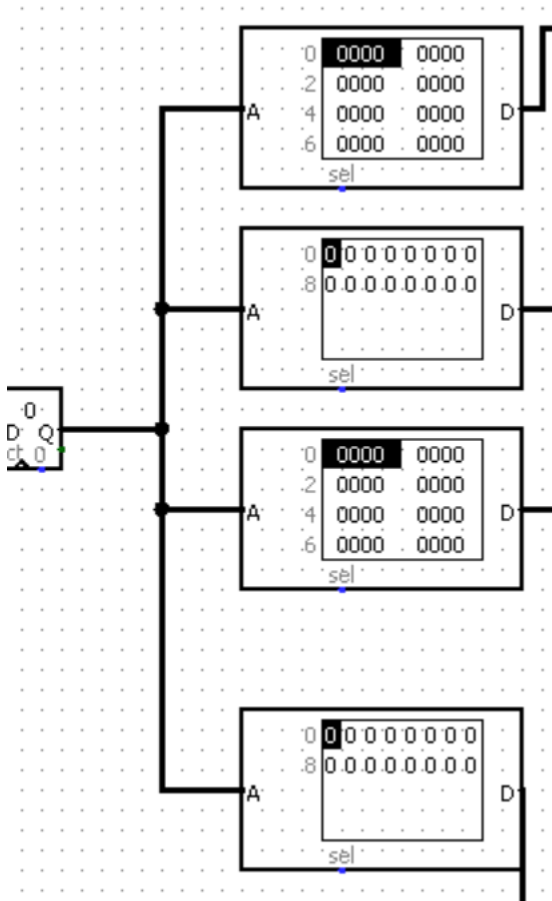
After taking counter, it was joined with 4 ROMs:



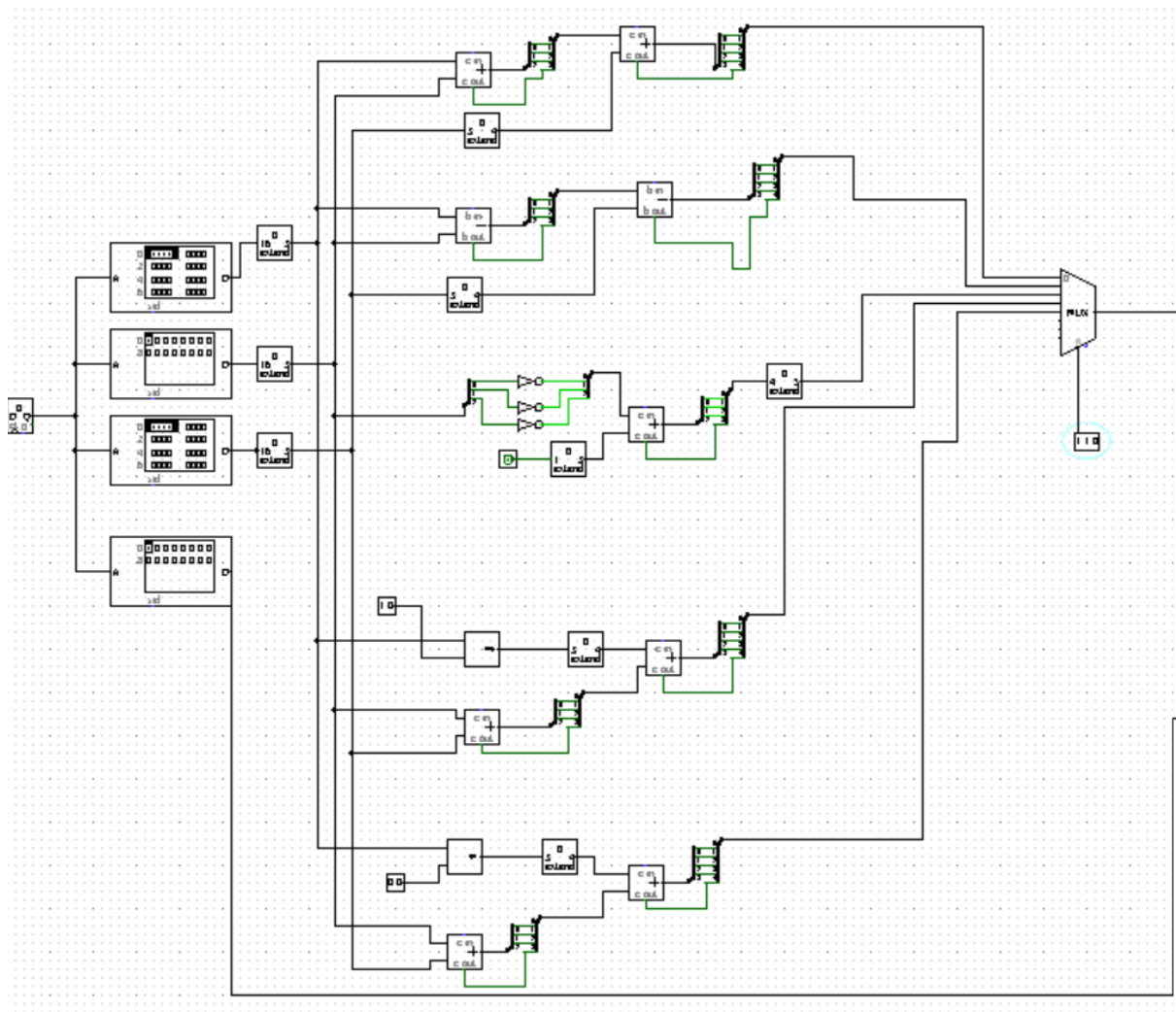The counter bit and 3 ROMs were then joined to previously built ALU



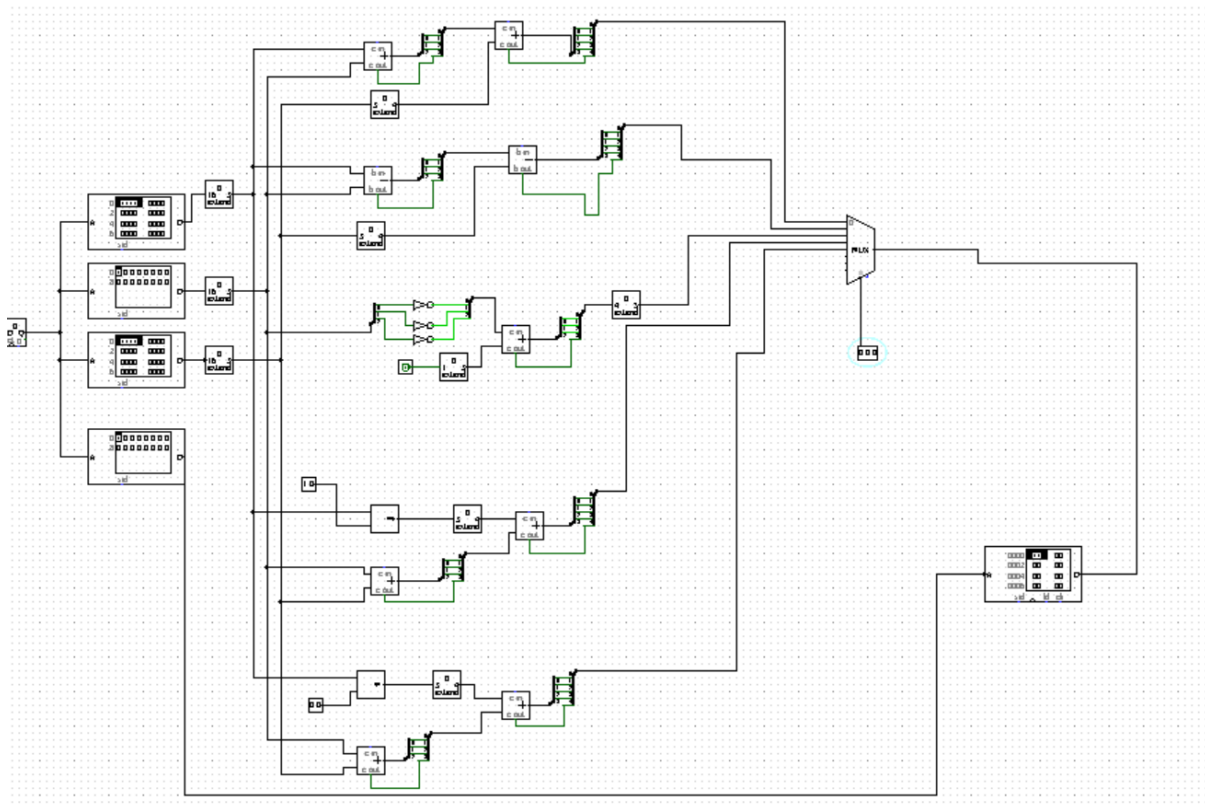After that , the output of ALU and the fourth ROM was joined to RAM



In this way, a general-purpose computer was developed by using the ALU previously built.

Logisim zip-file:



Logisim.zip